

# **Bahria University,**

## **Karachi Campus**



**LAB EXPERIMENT NO.**

**11**

### **LIST OF TASKS**

<b>TASK NO</b>	<b>OBJECTIVE</b>
<b>01</b>	<b>Design and implement the circuits for a half adder, full adder, half subtractor, and full subtractor in Multisim using basic gates, along with their truth tables and corresponding sum, difference, and carry/borrow equations.</b>
<b>02</b>	<b>Design and implement a 2-bit adder &amp; subtractor circuit in Multisim using basic gates.</b>
<b>03</b>	<b>Design and implement a 4-bit adder &amp; subtractor circuit in Multisim using Full Adder ICs.</b>
<b>04</b>	<b>Design and implement a 4-bit multiplier circuit in Multisim using Adder's ICs.</b>

**Submitted On:**

**Date: 5/12/2025**

**Task No. 01:**


“Design and implement the circuits for a half adder, full adder, half subtractor, and full subtractor in Multisim using basic gates, along with their truth tables and corresponding sum, difference, and carry/borrow equations.”

**Solution:****Half Adder:**

A ▼	B ▼	Sum ▼	Carry ▼
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$\text{Sum} = A'B + AB' = A \oplus B$$

$$\text{Carry} = A.B$$

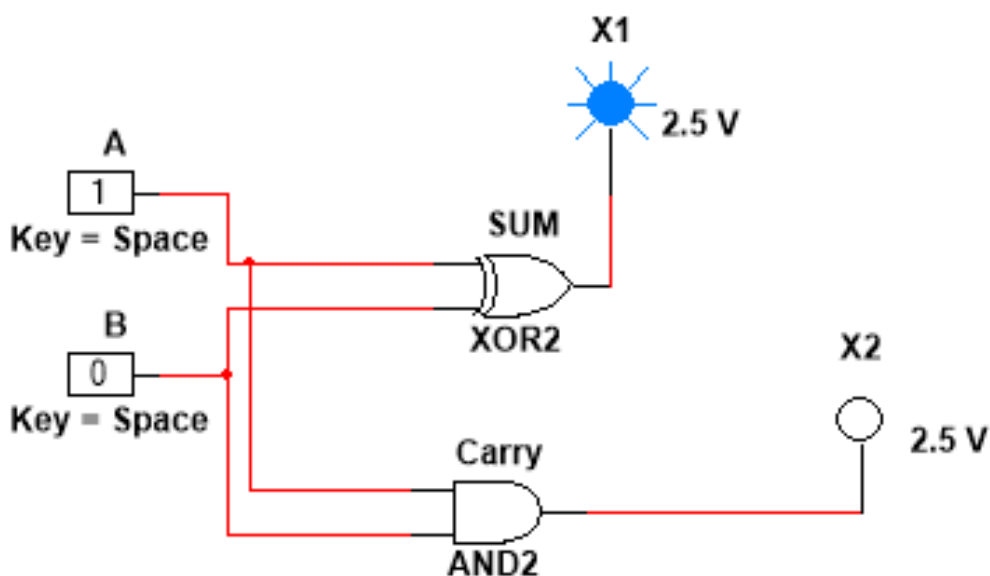


**Full Adder:**

A	B	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$\text{Sum} = A'B'C + A'BC' + AB'C' + ABC = A \oplus B \oplus C$$
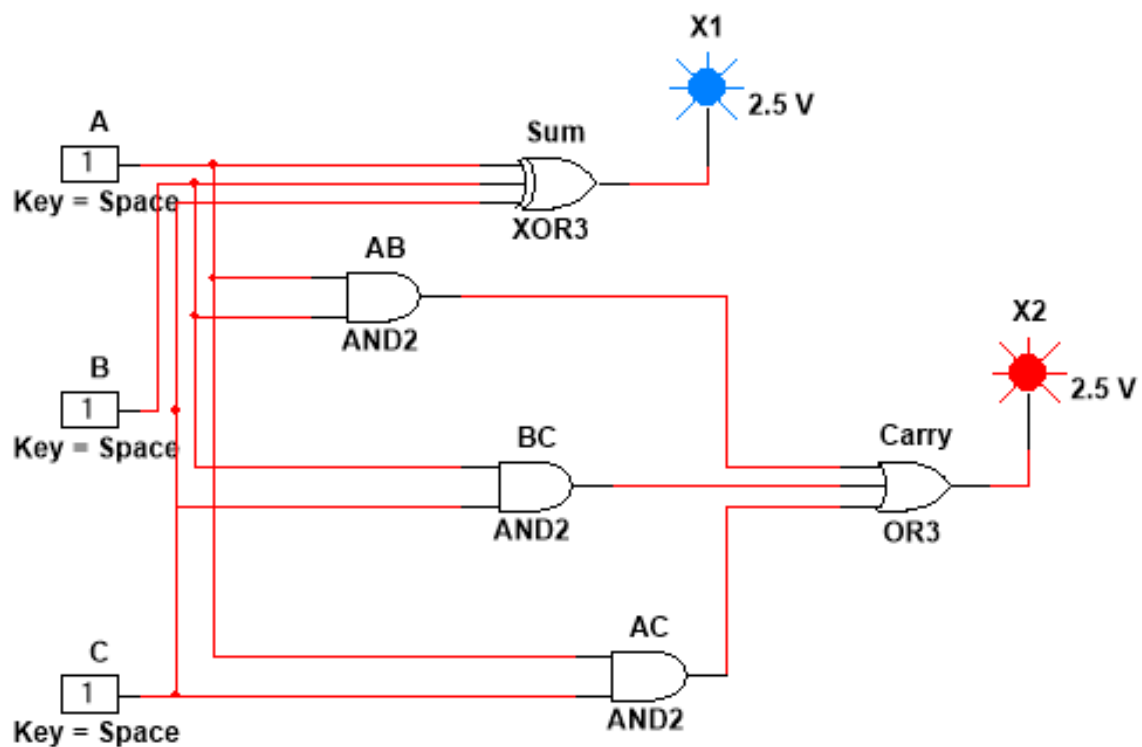
$$\text{Carry} = A'BC + AB'C + ABC' + ABC = AB + AC + BC$$




**Half Subtractor:**

A ▼	B ▼	Difference ▼	BorrowOut ▼
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

$$\text{Difference} = A'B + AB' = A \oplus B$$

$$\text{Borrow} = A'.B$$

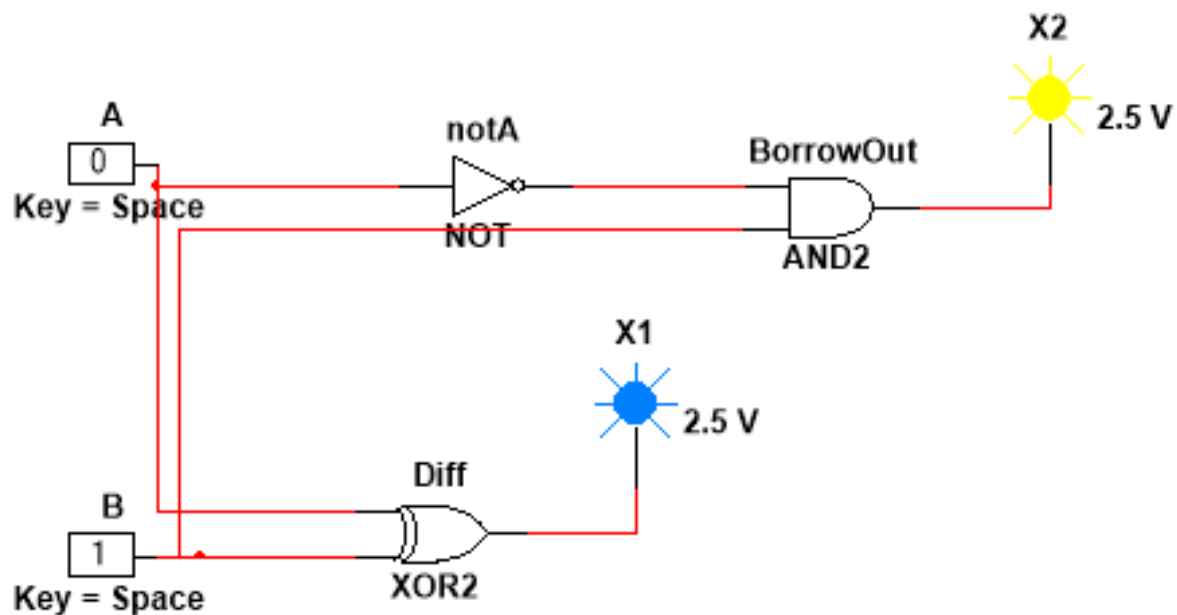


**Full Subtractor:**

A	B	Bin	Difference	Bout
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1



$$\text{Difference} = A'B'C + A'BC' + AB'C' + ABC = A \oplus B \oplus C$$
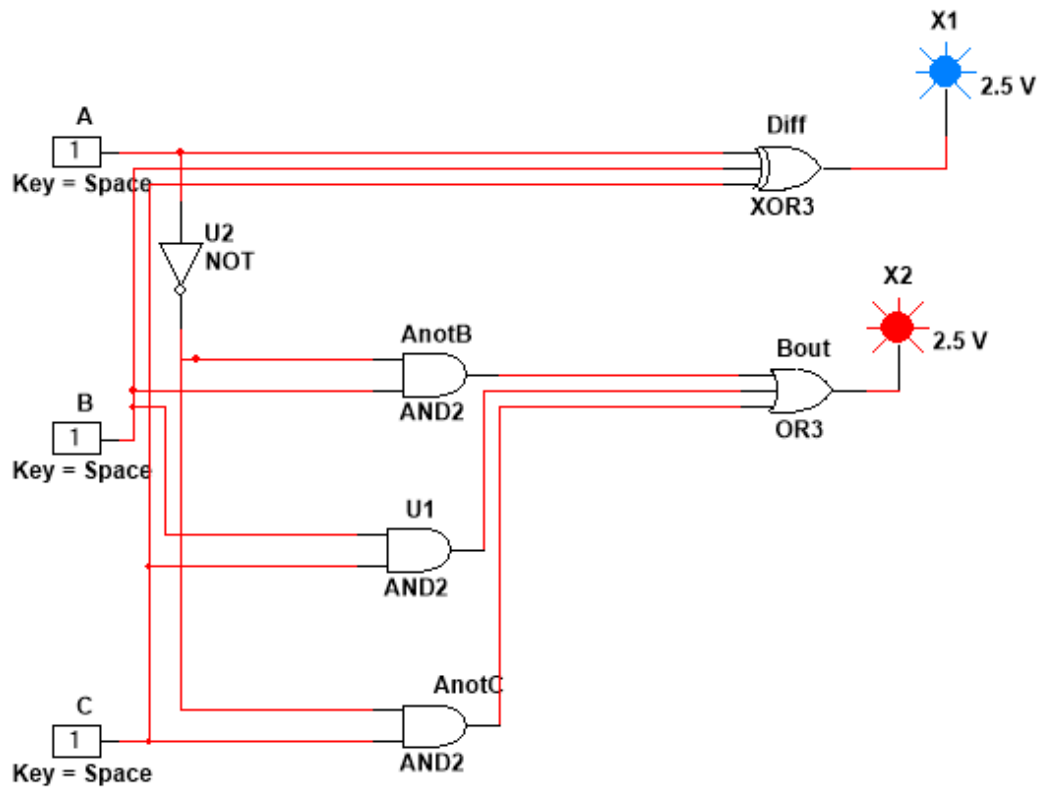
$$\text{Bout} = A'B'C + A'BC' + A'BC + ABC = A'B + A'C + BC$$





**Task No. 02:**

“Design and implement a 2-bit adder & subtractor circuit in Multisim using basic gates.”

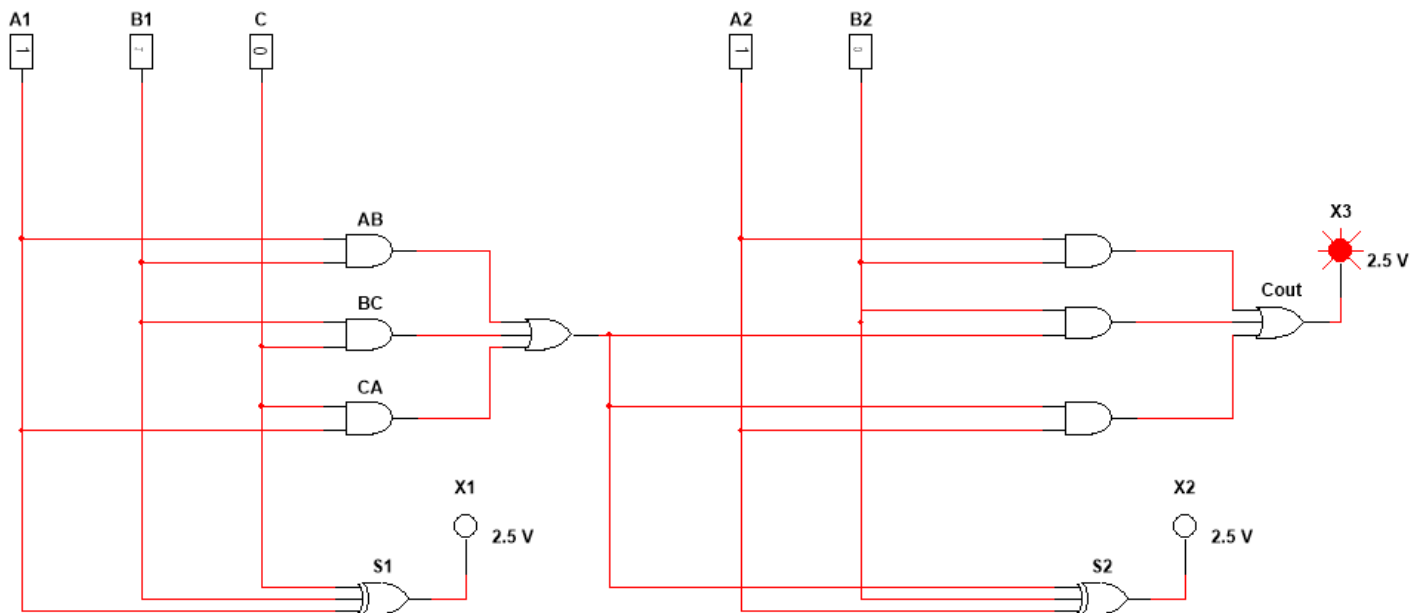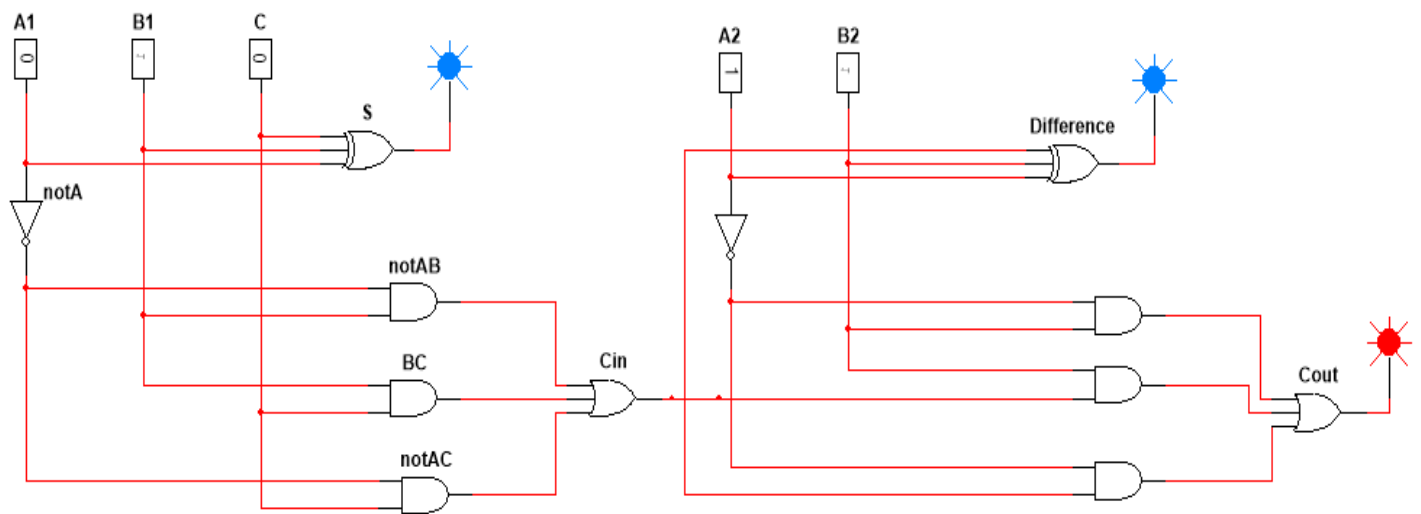**Solution:****2 BIT ADDER:****2 BIT SUBTRACTOR:**

**Task No. 03:**

“Design and implement a 4-bit adder & subtractor circuit in Multisim using Full Adder ICs.”

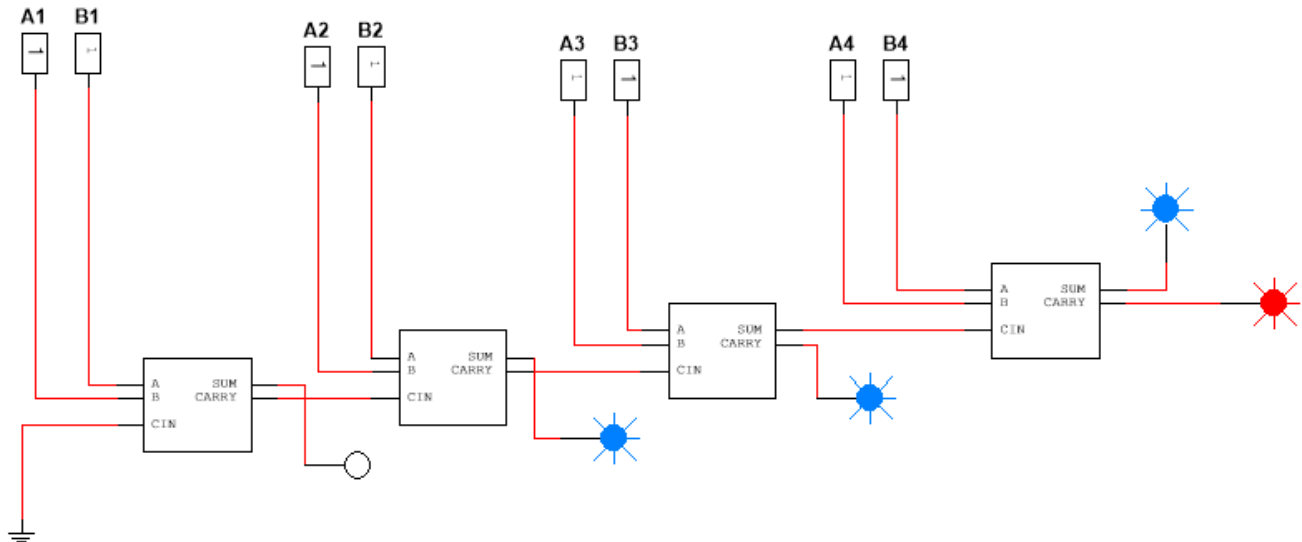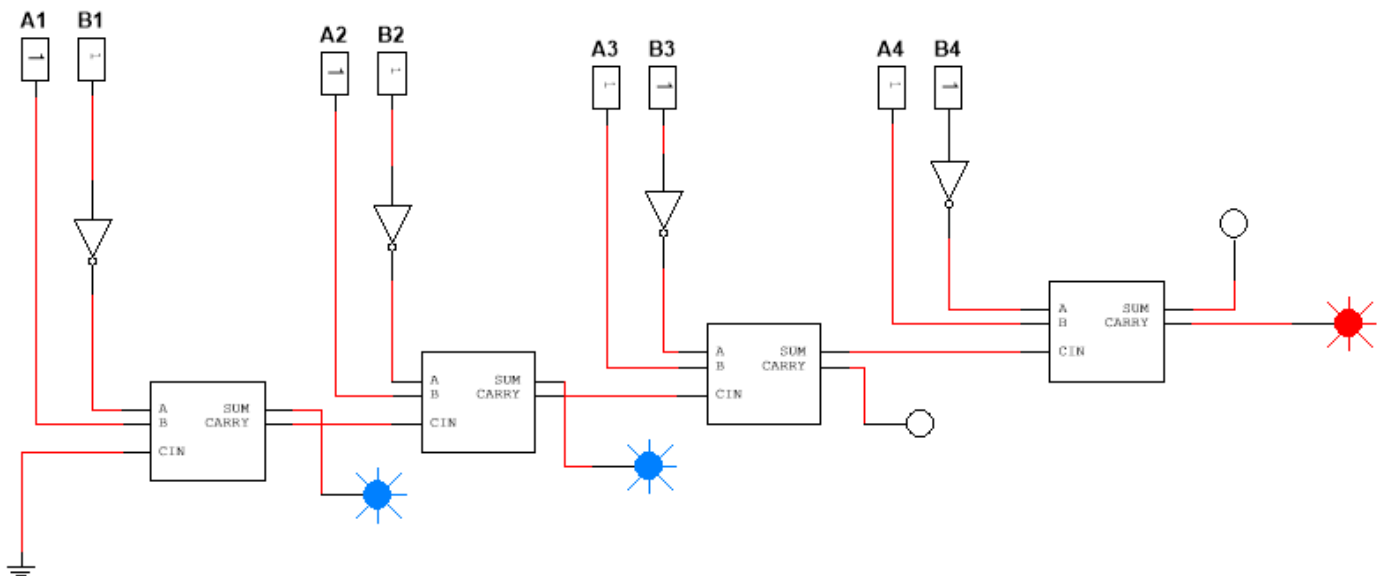**Solution:****4 BIT ADDER:****4 BIT SUBTRACTOR:**

**Task No. 04:**

“Design and implement a 4-bit multiplier circuit in Multisim using Adder’s ICs.”

**Solution:**

